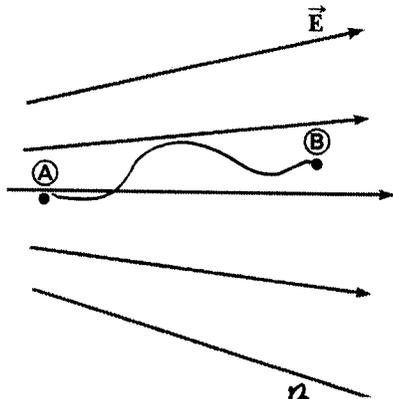


Name KEY

SP212R Exam 2

Points 100

1. Given the electric field below, the potential difference along a path from A to B is (5 pts):




- A. 0 V
- B. < 0 V
- C. > 0 V
- D. NOT ENOUGH INFORMATION

ANSWER B

WORK:

$$\Delta V = - \int_A^B \vec{E} \cdot d\vec{s} = \text{since } \vec{E} \cdot d\vec{s} > 0 \Rightarrow \Delta V < 0$$

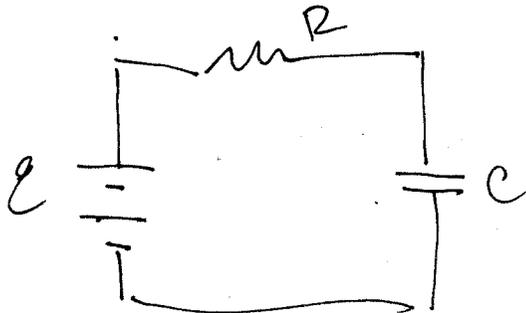2. An RC circuit consists of a 50.0 kΩ resistor in series with a 20.0 μF capacitor, both connected to a 25.0 V emf. At what time will the current be at 75% of its maximum? (10 pts)



$$I = \frac{\epsilon}{R} e^{-t/\tau}$$

$$\tau = RC$$

$$0.75 I = \frac{\epsilon}{R} e^{-t/\tau}$$


$$e^{-t/\tau} = 3/4$$

$$-t/\tau = \ln(0.75)$$

$$t = -RC \ln(0.75) = (50.0 \times 10^3 \Omega)(20.0 \times 10^{-6} \text{ F}) \ln 0.75$$

$$t = 0.295 \text{ s}$$

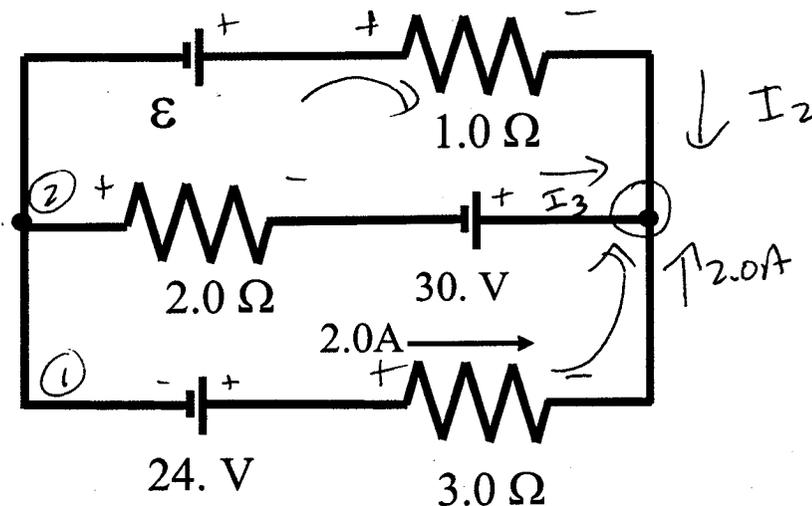3. Given the following DC circuit as sketched (25 points):



Label currents and then write the necessary Kirchoff Law Equations to solve this circuit here. Then answer the following questions:

$$1) \quad 2.0\text{A} + I_2 + I_3 = 0$$

$$\textcircled{1} \quad -30.0\text{V} + I_3(2.0\Omega) + 24.0\text{V} - (2.0\text{A})(3.0\Omega) = 0$$

$$\textcircled{2} \quad \mathcal{E} - I_2(1.0\Omega) - 30.0\text{V} + I_3(2.0\Omega) = 0$$

a. What is the current in the 2.0 Ω resistor? (5)

Solve $\textcircled{1}$: $I_3(2.0\Omega) = (2.0\text{A})(3.0\Omega) - 24.0\text{V} + 30.0\text{V} =$

$$\boxed{I_3 = 2.0\text{A}} \quad (\text{the } 2.0\text{A} \text{ is to the left})$$

b. What is the current in the 1.0 Ω resistor? (5)

Solve 1): $2.0\text{A} + I_2 + I_3 = 0 \Rightarrow I_2 = -2.0\text{A} - I_3 = -2.0\text{A} - 2.0\text{A} = -4.0\text{A}$

$$I_2 = \frac{2.0\text{A} - 8.0\text{A}}{-1} = 6.0\text{A} \quad (\text{i.e. opposite direction})$$

c. What is the top battery electromotive force, ε? (5)

Solve $\textcircled{2}$: $\mathcal{E} = I_2(1.0\Omega) + 30.0\text{V} - I_3(2.0\Omega) = (6.0\text{A})(1\Omega) + 30.0\text{V} - (2.0\text{A})(2.0\Omega)$

$$\mathcal{E} = 10.0\text{V} + 30.0\text{V} - 4.0\text{V} = 36.0\text{V}$$

d. What is the power dissipated in the 3 Ω resistor? (5)

$$P = I^2 R = (2.0\text{A})^2(3.0\Omega) = 12\text{W}$$


- e. The $3\ \Omega$ resistor is a cylinder with length of 1 cm and a cross section of $0.0013\ \text{m}^2$. What is the resistivity of the material in the resistor? (5)

$$R = \frac{\rho l}{A} \Rightarrow \rho = \frac{RA}{l} = \frac{(3\ \Omega) \cdot (0.0013\ \text{m}^2)}{0.01\ \text{m}} = 0.39\ \Omega \cdot \text{m}$$

$\rho = 0.39\ \Omega \cdot \text{m}$

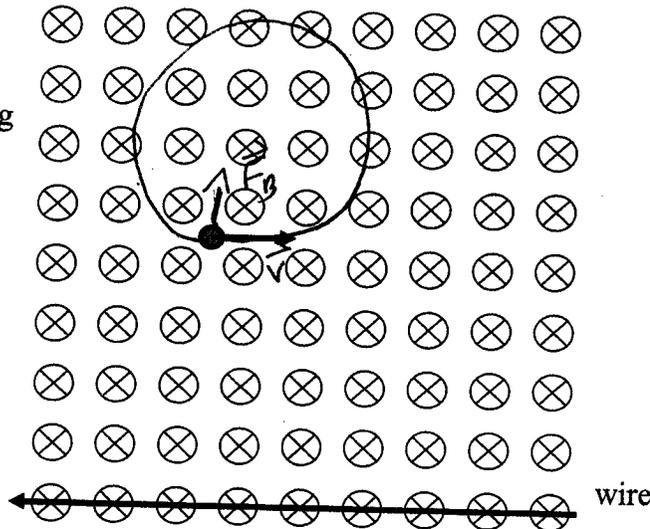4. A proton is traveling at $5.0 \times 10^5\ \text{m/s}$ in a direction perpendicular to a uniform magnetic field with magnitude $0.0050\ \text{T}$, directed into the page (20 points).

$m_p = 1.67 \times 10^{-27}\ \text{kg}$
 $e = 1.6 \times 10^{-19}\ \text{C}$



- a. Sketch the path of the proton. The magnetic field can be made bigger if needed to complete the path(5)

- b. What is the radius of the path? (5)

$$F_B = qvB = \frac{mv^2}{r} \Rightarrow r = \frac{mv}{qB} = \frac{(1.67 \times 10^{-27} \text{ kg})(5.0 \times 10^5 \text{ m/s})}{(1.60 \times 10^{-19} \text{ C})(0.0050 \text{ T})}$$

$$r = 1.04 \text{ m}$$

- c. What is the period of the circular motion? (Hint: The period is the time it takes to make one complete circle, i.e., travel a distance equal to the circumference) (5)

$$T = \frac{2\pi r}{v} = \frac{2\pi(1.04 \text{ m})}{5.0 \times 10^5 \text{ m/s}} = 1.31 \times 10^{-5} \text{ s}$$

- d. A wire at the bottom of the field is used to supply power to the system that creates the protons (the system not shown). The wire carries a current of 5.0 A and is 20.0 cm long. What is the magnitude and direction of the force on the wire? (5)


$$\vec{F} = I\vec{l} \times \vec{B} \Rightarrow \text{downward}$$

$$F = IlB = (5.0 \text{ A})(0.2 \text{ m})(0.0050 \text{ T})$$

$$\boxed{5 \text{ mN}}$$

5. A long straight walled cylindrical shell (hollow and very thin) with a radius of 10.0 cm carries a current $I_0 = 5.0$ A to the right. Along the longitudinal axis of the cylinder is a thin wire with a current of I_0 to the left. (10 points)

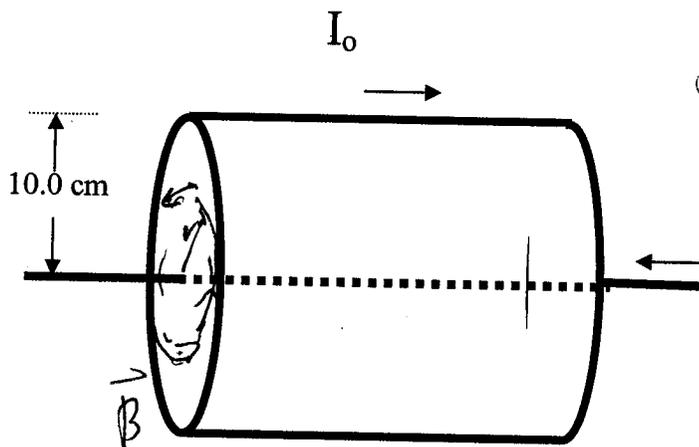a. Use Ampere's law to find an expression for the magnetic field at a distance of 5.0 cm from the inner wire. Sketch the direction of this field. (5)




$$\oint \vec{B} \cdot d\vec{s} = \mu_0 I_{enc} l$$

$$B = \frac{\mu_0 I_0}{2\pi r}$$

$$= \frac{(4\pi \times 10^{-7}) (5.0 \text{ A})}{2\pi (0.05 \text{ m})}$$

$$= 2.0 \times 10^{-5} \text{ T}$$

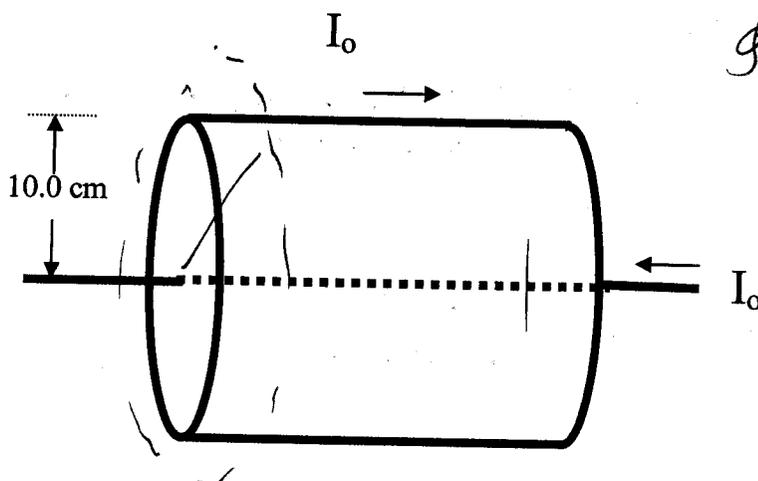b. Use Ampere's law to find an expression for the magnetic field at a distance of 15.0 cm from the inner wire. Sketch the direction of this field. (5)




$$\oint \vec{B} \cdot d\vec{s} = \mu_0 I_{enc} l$$

$$I_{enc} = 0$$

$$\Rightarrow \underline{B = 0}$$

For any partial credit, be sure you start with Ampere's Law and clearly show the path around which you are integrating.

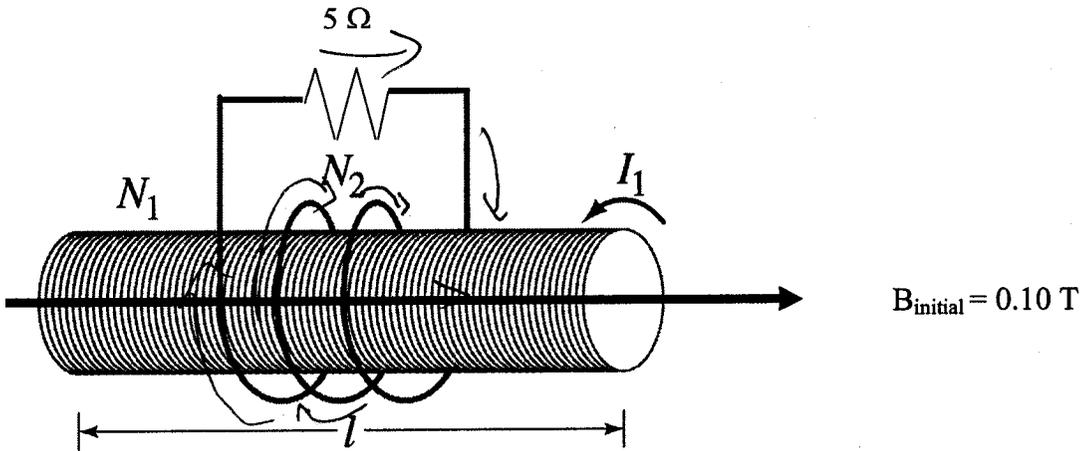6. An ideal solenoid shown in the center has a cross-sectional area of 0.0050 m^2 . Initially, the magnetic field caused by the current shown in the solenoid is 0.10 T . (20 points)



- a. If the number of turns in the solenoid, $N_1 = 100$ and the length of the solenoid, $l = 5.0 \text{ cm}$, what current, I_1 , is necessary to cause the initial magnetic field of 0.10 T . (5)

$$B_{\text{sol}} = \mu_0 n I \Rightarrow I = \frac{B}{\mu_0 \left(\frac{N}{l}\right)} = \frac{0.10 \text{ T}}{(4\pi \times 10^{-7}) \left(\frac{100}{0.05 \text{ m}}\right)}$$

$$I = 40.0 \text{ A}$$

- b. In a period of 0.020 seconds the current, I_1 , increases and the field becomes 0.50 T . What is the change in magnetic flux in the solenoid during these 0.020 seconds? (5)

$$\Phi_B = \int \vec{B} \cdot d\vec{A} = BA$$

$$\Delta \Phi_B = (B_f - B_i)A = (0.50 - 0.10 \text{ T}) (0.0050 \text{ m}^2)$$

$$= 2.0 \times 10^{-3} \text{ T} \cdot \text{m}^2$$

- c. What average electromotive force (voltage) is induced in a larger **two-turn** ($N_2 = 2$) coil with cross section 0.015 m^2 surrounding the smaller solenoid as shown during this 0.020 seconds? (5)

$$\left| \mathcal{E} \right| = \left| \frac{N_2 \Delta \Phi_B}{\Delta t} \right| = \left| (2) \left(\frac{2.0 \times 10^{-3} \text{ T} \cdot \text{m}^2}{0.020 \text{ s}} \right) \right| = 0.20 \text{ V}$$

- d. The larger coil is connected to a 5.0Ω resistor as shown (ignore the resistance of the coil wire). What is the magnitude **and direction** of the current in the resistor while the magnetic field is changing? (5)


$$I = \frac{\mathcal{E}}{R} = \frac{0.20 \text{ V}}{5 \Omega} = 0.04 \text{ A to right}$$

7. RL circuits and LC circuits (10 pts):

a) What is the inductance of a series RL circuit in which $R = 1.0 \text{ K}\Omega$ if the current increases to one-third of its final value in $30 \mu\text{s}$ (5 pts)?

- a. 74 mH
- b. 99 mH
- c. 49 mH
- d. 62 mH
- e. none of the above

Answer: A

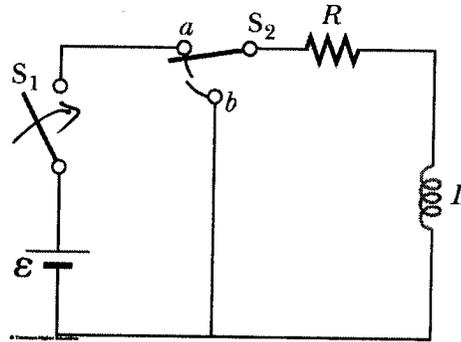

$$I = \frac{\mathcal{E}}{R} (1 - e^{-t/\tau}) ; \tau = L/R$$

$$0.33 \frac{\mathcal{E}}{R} = \frac{\mathcal{E}}{R} (1 - e^{-t/\tau}) \Rightarrow 0.33 = (1 - e^{-t/\tau})$$


$$-e^{-t/\tau} = -0.666 = -2/3$$

$$\Rightarrow \tau = \frac{L}{R} = \frac{-t}{\ln(2/3)} ; L = (1.0 \times 10^3 \Omega) (30 \times 10^{-6} \text{ s}) / \ln(2/3) = 74.0 \text{ mH}$$

b) A series LC circuit contains a 100 mH inductor, a 36.0 mF capacitor that was charged with a 12 V battery. The frequency of the electromagnetic oscillations in the circuit is (5 pts)

- a. $5.73 \times 10^{-4} \text{ Hz}$.
- b. $9.55 \times 10^{-3} \text{ Hz}$.
- c. 0.442 Hz.
- d. 2.66 Hz.
- e. 44.0 Hz.

Answer: D

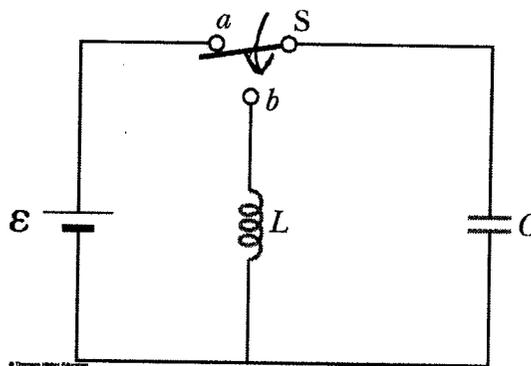

$$\omega = \sqrt{\frac{1}{LC}}$$

$$= \sqrt{\frac{1}{(36.0 \times 10^{-3} \text{ F})(100 \times 10^{-3} \text{ H})}} = 16.7 \text{ rad/s}$$

$$f = \frac{\omega}{2\pi} = \frac{16.7 \text{ rad/s}}{2\pi} = 2.65 \text{ Hz}$$