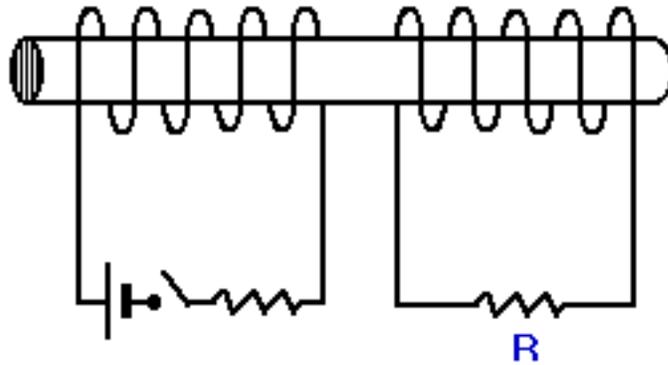


**CPS lesson**  
**Induction and AC Circuits**  
**ANSWER KEY**

1.


For a short time after the switch is closed, the current through resistor R is:



- \* A. to the left
- B. to the right
- C. zero

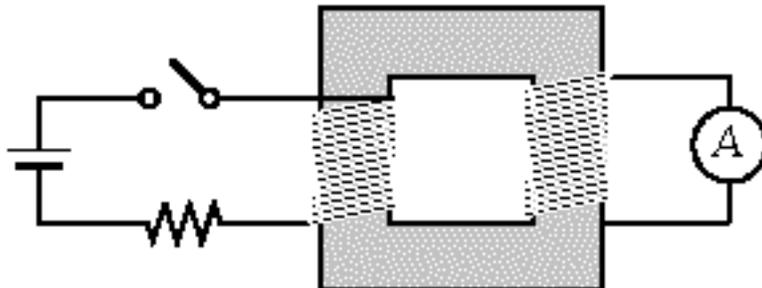2.

After the switch is closed, the ammeter shows:




- A. zero current always
- B. a steady nonzero current

- \* C. a nonzero current which quickly fades away


3. A rectangular loop of wire is pushed toward a long straight current-carrying wire.

The induced current in the loop is:

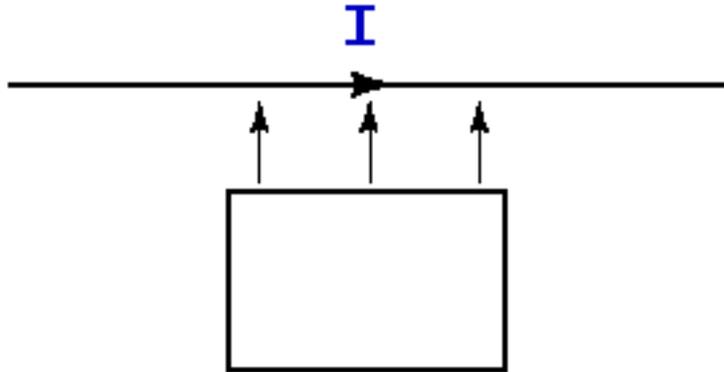


- A. clockwise
- \* B. counter-clockwise
- C. zero

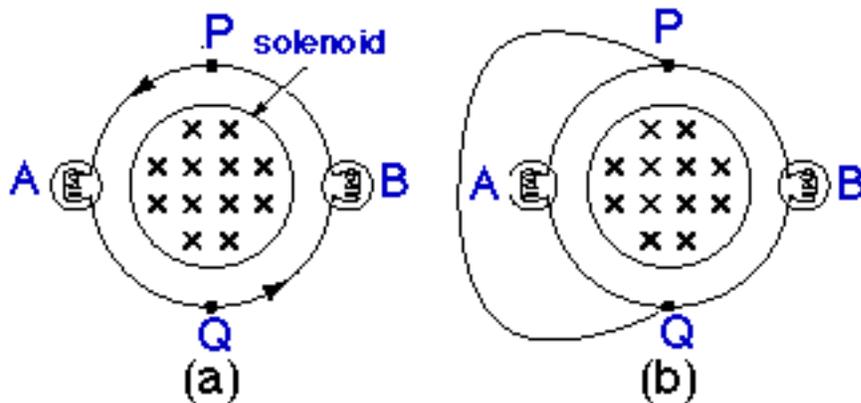4. A solenoid produces a magnetic field whose strength is increasing into the page. The induced emf in a loop around the wire lights up the bulbs in (a). What happens to the bulbs when points P and Q are shorted as in (b)?




- \* A. A goes out, B brightens
- B. B goes out, A brightens
- C. A goes out, B dims
- D. B goes out, A dims

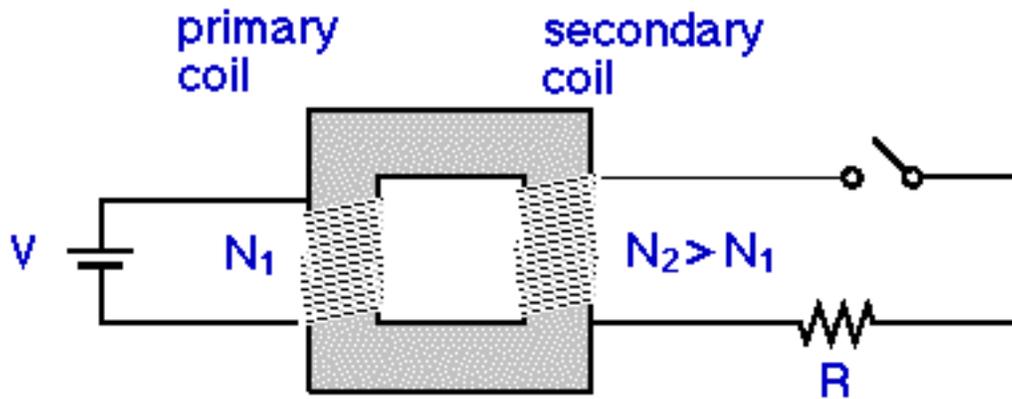5.  
After the switch is closed, the voltage across the resistor R is:



- A.  $V N_2 / N_1$
- B.  $V N_1 / N_2$
- C.  $V$
- \* D. zero

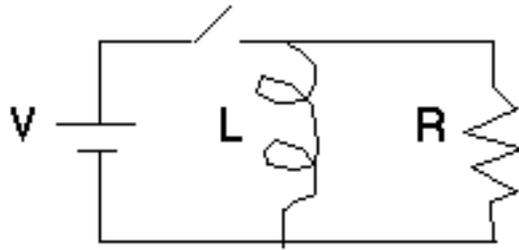6. The switch is closed for a long time, so that current  $I$  is steadily flowing through the inductor. If the switch is opened, the voltage across the resistor is now:




A. always zero

B. constantly V

\* C. initially IR but fades away to zero

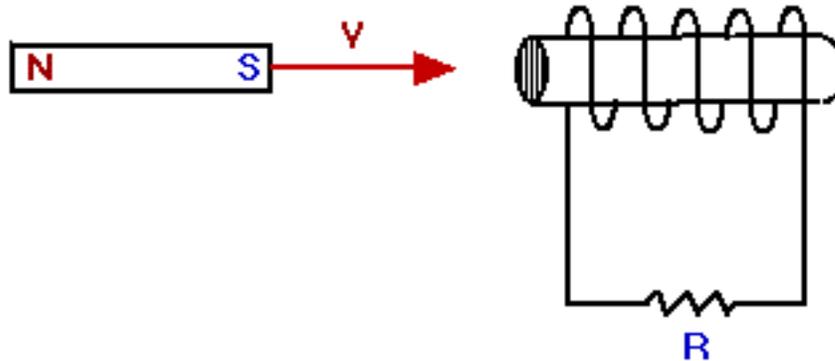7.

As the magnet is moved toward the coil, the current through resistor R is:



\* A. to the left

B. to the right

C. zero

8.

Two current-carrying coils are near one another. We can increase the mutual inductance of the pair by:

A. moving the coils closer to each other

- B. increasing the currents in the coils
- C. increasing the number of turns in the coils
- \* D. doing two of the above
- E. doing all three of the above

9.

In transmitting electricity from a power plant to a home, what are transformers used for?

- A. to step up the output voltage at the power plant
- B. to step down the input voltage to the house
- \* C. both of the above
- D. neither of the above

10.

The magnetic energy stored in an inductor is proportional to:

- A. the square of the current in the inductor
- B. the square of the magnetic field through the inductor
- \* C. both of the above
- D. neither of the above

11.

Which statement is true?

- \* A. Induced electric field lines form closed loops.
- B. Induced electric field is conservative.

- C. Both of the above are true.
- D. Neither of the above are true.

12.

Where is emf induced in a transformer?

- A. output voltage of the secondary
- B. back emf at the primary
- C. eddy currents in the iron core
- D. in two of the above
- \* E. in all three of the above

13.

Which of the following have self-inductance?

- A. solenoid
- B. toroid
- C. wire loop
- D. straight wire
- \* E. all of the above

14. A conducting disc swings on a pendulum through the gap of a c-shaped magnet.

Which type of disc damps out the motion most rapidly?

- \* A. a solid disc

B. a disc which has slots cut into it

15.

Self-inductance of a coil depends upon:

A. magnetic flux through and current in the coil

\* B. number of turns and cross-sectional area of the coil

C. both A and B

D. neither A nor B

16.

A resistor is connected across an ac emf  $e$ . The resulting current:

A. leads the emf

B. lags the emf

\* C. is in phase with the emf

D. The answer depends upon the frequency of the emf.

17.

A capacitor is connected across an ac power supply. As the frequency is increased, the peak current in this circuit:

\* A. increases

B. decreases

C. remains the same

18.

In a dc circuit, which element has the greatest resistance to charge flow?

- \* A. capacitor
- B. inductor
- C. resistor
- D. The answer depends on the values of C, L, and R.

19. A capacitor having initial charge  $Q$  is connected across an inductor. The energy of the inductor is a maximum when the charge on the capacitor is:


- A.  $Q$
- B.  $Q/2$
- \* C. zero
- D. The energy of the inductor is time-independent.

20. An initially charged capacitor is connected in series with an inductor having a small resistance. As a function of time, the charge on the capacitor:

- A. oscillates sinusoidally with constant amplitude
- \* B. oscillates sinusoidally with decreasing amplitude
- C. monotonically decreases to zero
- D. remains constant because there is no driving emf

21. The magnetic flux through the loop is:

(a)

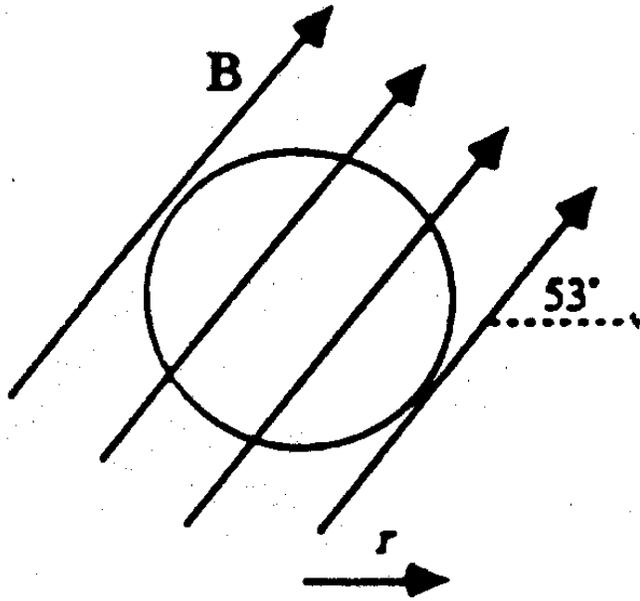

The loop and the magnetic field are both in the plane of the paper.

A.  $B \pi r^2$

\* B. zero

C.  $B \pi r^2 \cos(53^\circ)$

$\pi r^2$

$B \pi r^2$

$B \pi r^2$

$B \pi r^2 \cos(53^\circ)$


D.  $B \pi r^2 \cos(37^\circ)$

$B \pi r^2 \sin(53^\circ)$

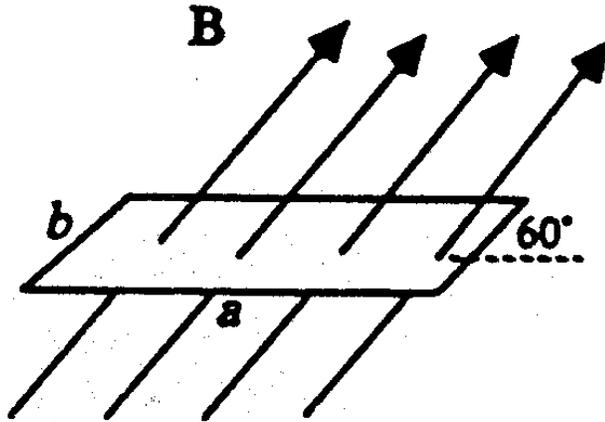22. The magnetic flux through the loop is:

(b)

The rectangular loop is perpendicular to the page and the magnetic field is in the plane of the paper.




- A.  $B ab$
- B. zero
- C.  $B ab \cos(60^\circ)$
- \* D.  $B ab \cos(30^\circ)$

23. The magnetic flux through the loop is:

(c)

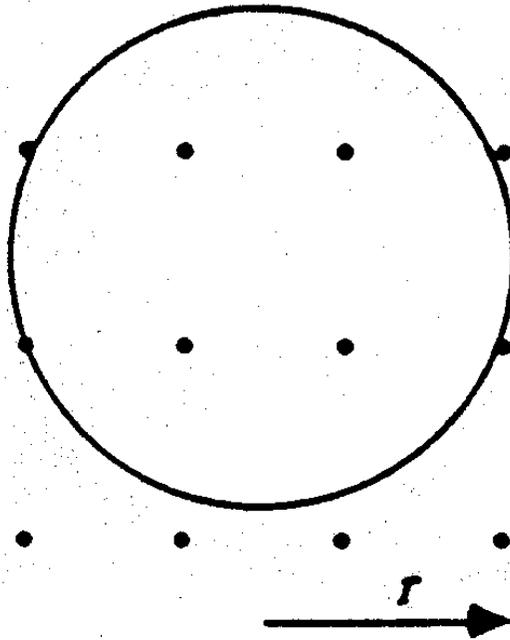**B out of paper**


The loop is in the plane of the paper and the field is perpendicular to the paper.



- \* A.  $B \pi r^2$   
B. zero  
C.  $B 2\pi r$   
D. none of the above

24. The magnetic flux through the loop is:


(d) The field is parallel to side **a**.

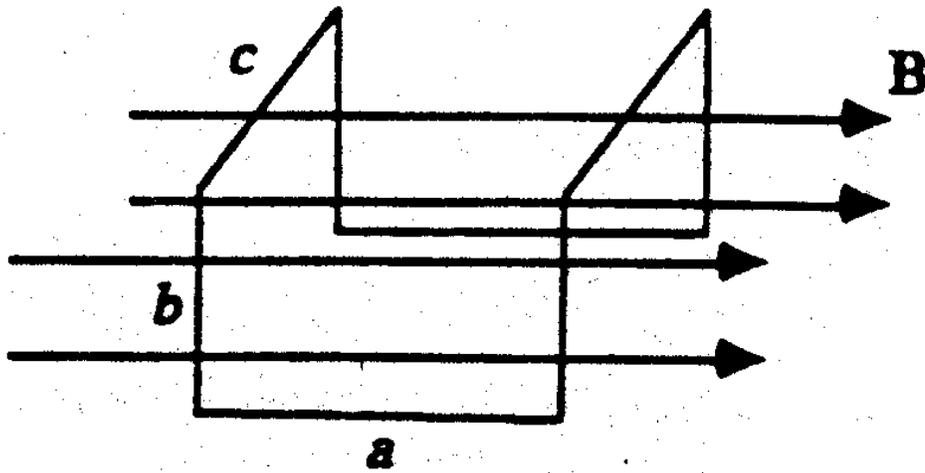

- A.  $2B ab$
- \* B. zero
- C.  $2B bc$
- D.  $B ac$

25. The magnetic flux through the loop is:


(c) The field is parallel to side b.

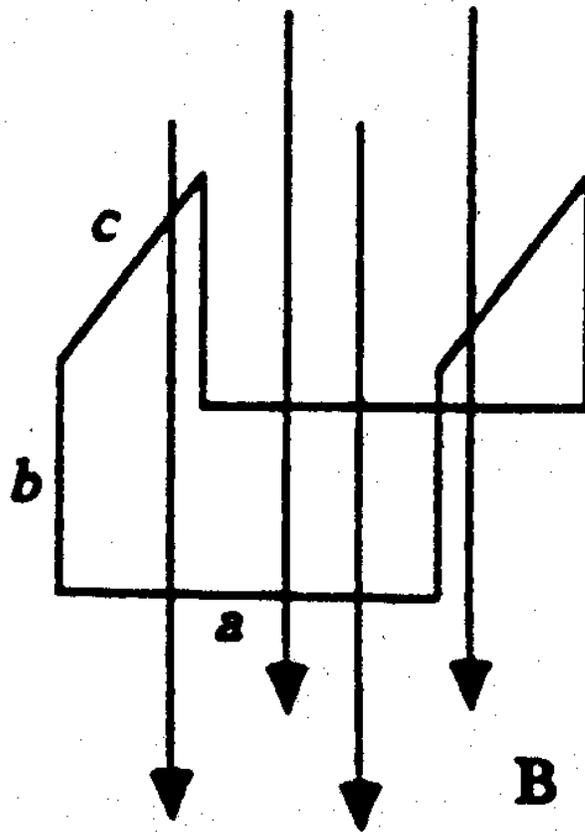

- A.  $2B ab$
- B. zero
- C.  $2B bc$
- \* D.  $B ac$

26. The magnetic flux through the loop is:


(f) The field is parallel to side c.

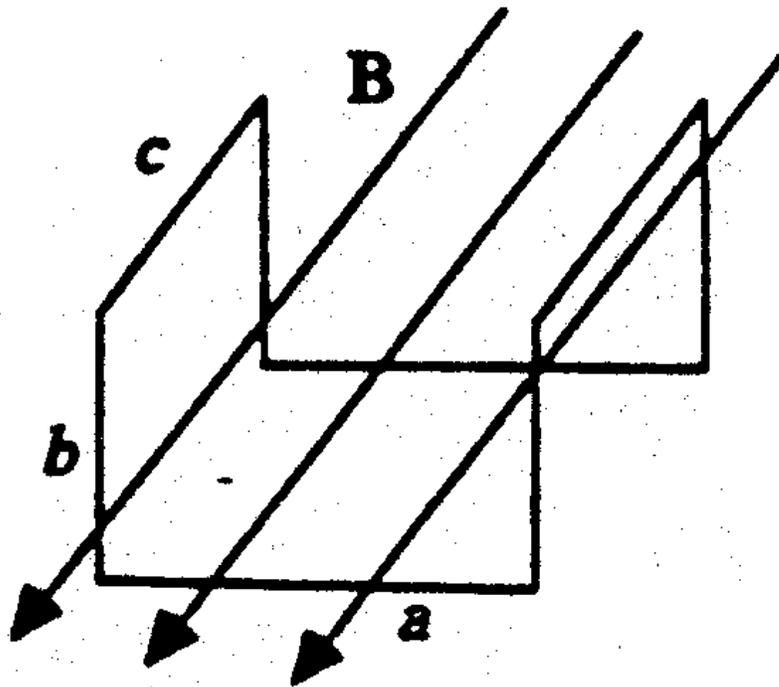

- A.  $2B ab$
- \* B. zero
- C.  $2B bc$
- D.  $B ac$

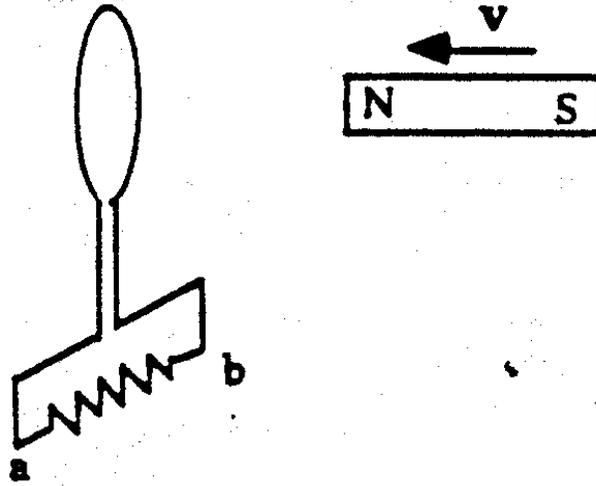27. The induced current in the resistor is:


A magnet in the plane of the paper moves toward the fixed loop that is perpendicular to the paper.



- \* A. from a to b
- B. from b to a
- C. zero
- D. it depends

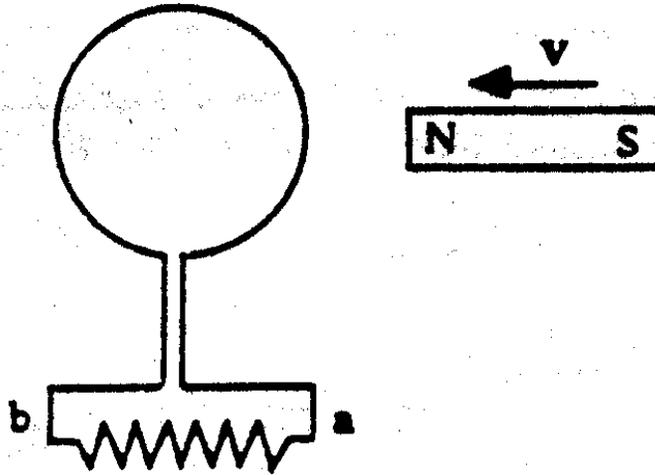28. The induced current in the resistor is:


A magnet in the plane of the paper moves toward a fixed loop that is also in the plane of the paper.



- A. from a to b
- B. from b to a
- \* C. zero
- D. it depends

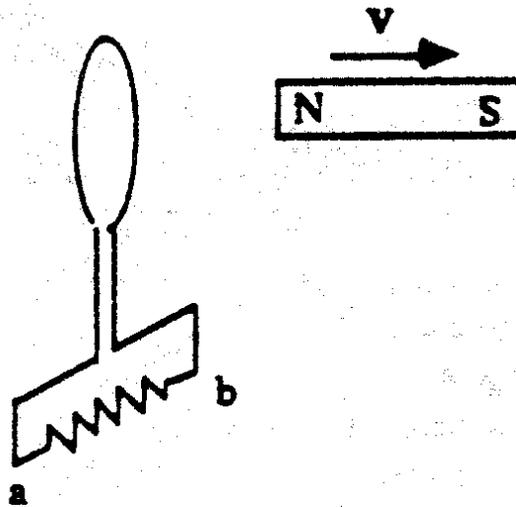29. The induced current in the resistor is:


A magnet in the plane of the paper moves away from a fixed loop that is perpendicular to the plane of the paper.



- A. from a to b
- \* B. from b to a
- C. zero
- D. it depends

30. The induced current in the resistor is:

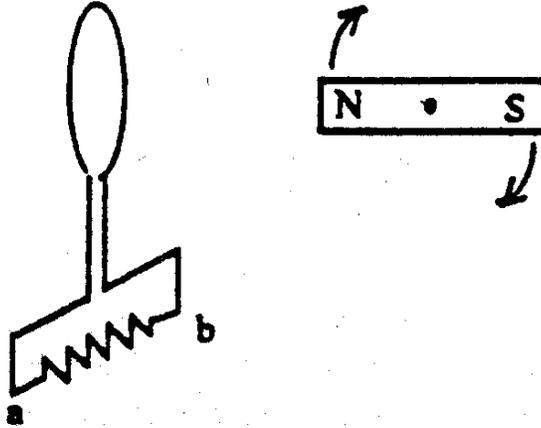
(d) A magnet in the plane of the paper is rotated about its center so that the North pole and South pole exchange positions relative to a fixed loop that is perpendicular to the plane of the paper.



- A. from a to b
- \* B. from b to a
- C. zero
- D. it depends

31. The induced current in the resistor is:

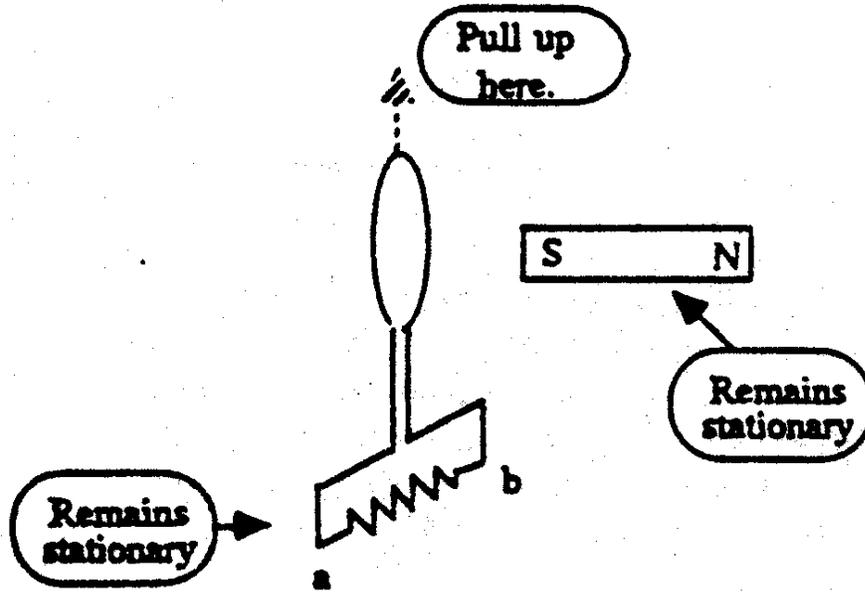
(e) A magnet in the plane of the paper is held fixed as a loop perpendicular to the plane and originally open is stretched vertically so its opposite sides come together.



- \* A. from a to b
- B. from b to a
- C. zero
- D. it depends

32. The induced current in the resistor is:

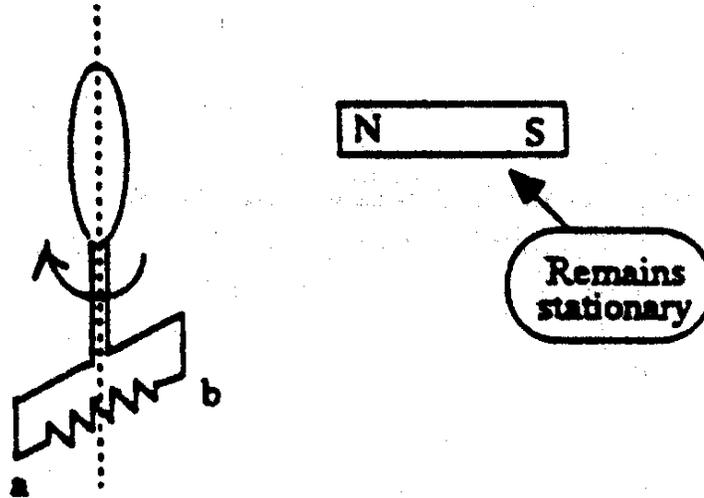
(f) A magnet in the plane of the paper is held fixed as a loop originally perpendicular to the plane of the paper, is rotated clockwise into the plane of the paper.



- A. from a to b
- B. from b to a
- C. zero
- D. it depends

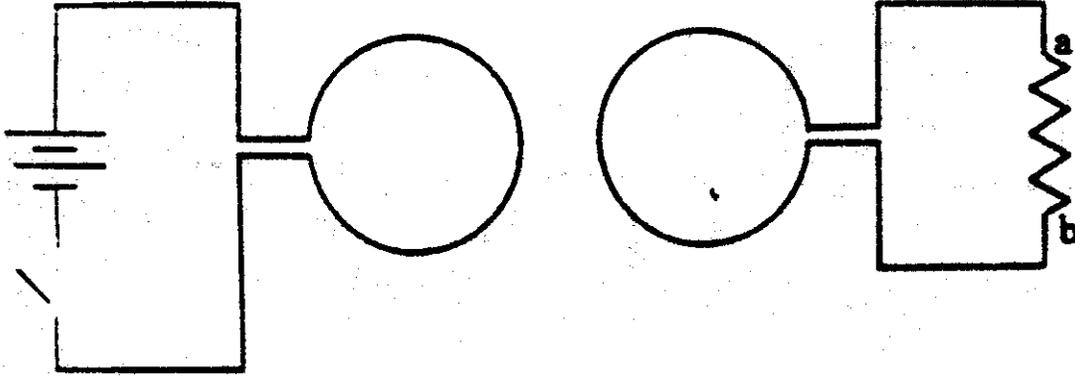33. The induced current in the resistor is:


) The switch on the left is closed. (This is similar to the ignition system on a car.)



- \* A. from a to b
- B. from b to a
- C. zero
- D. it depends

34. The induced current in the resistor is:

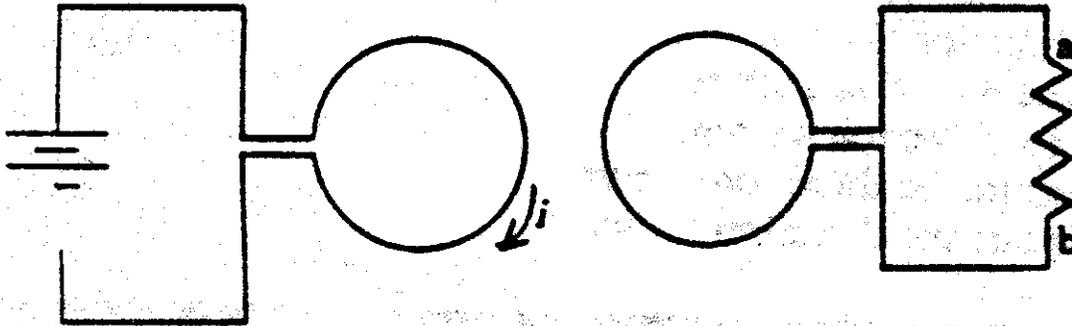
b) A steady clockwise current flows in the circuit on the left.



- A. from a to b
- B. from b to a
- \* C. zero
- D. it depends

35. The induced current in the resistor is:

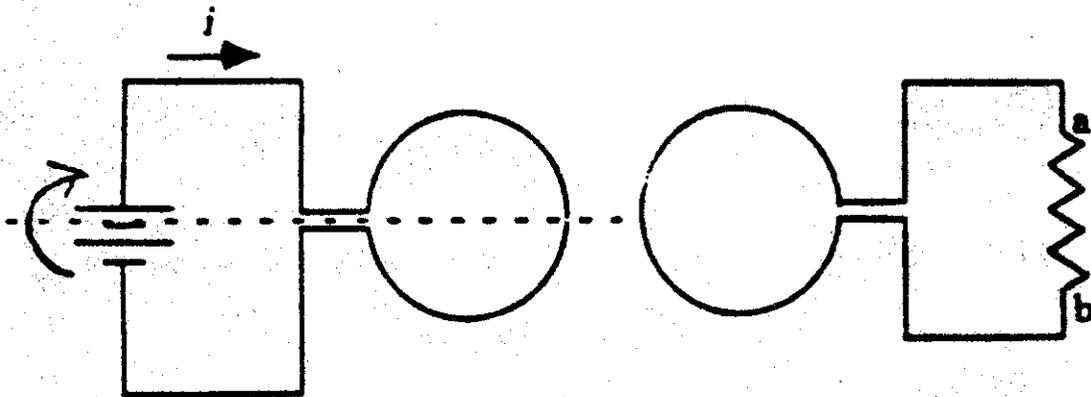
(c) The circuit on the left is rotated 90° about a horizontal axis.



- A. from a to b
- \* B. from b to a
- C. zero
- D. it depends

36. The induced current in the resistor is:

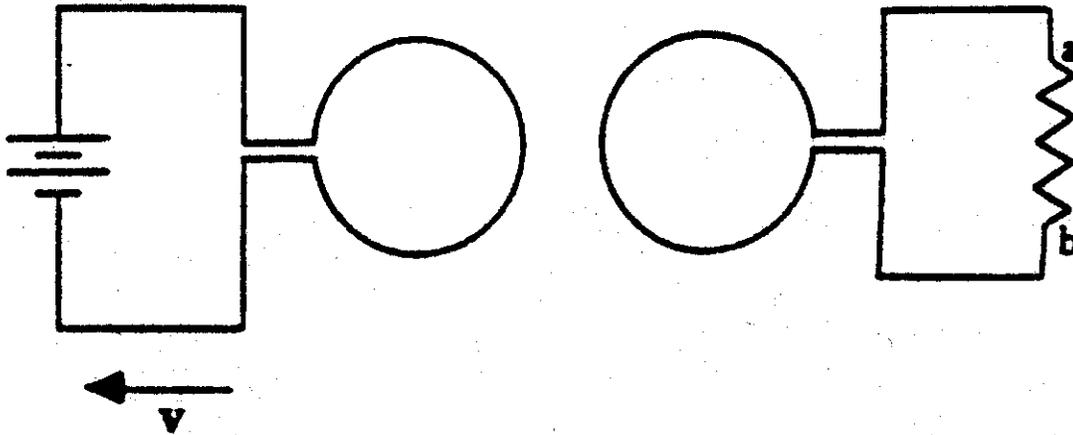
(d) The circuit on the left is moved away from the one on the right.



- A. from a to b
- \* B. from b to a
- C. zero
- D. it depends

37. The induced current in the resistor is:

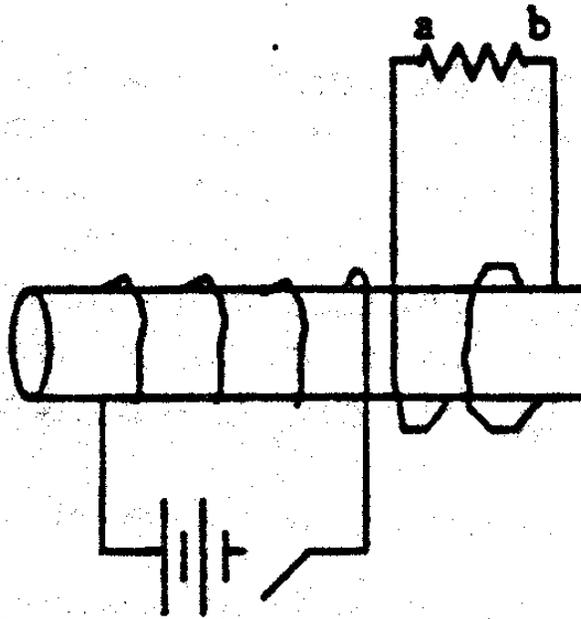
(e) The switch on the bottom circuit is closed.



- \* A. from a to b
- B. from b to a
- C. zero
- D. it depends

38. The induced current in the resistor is:

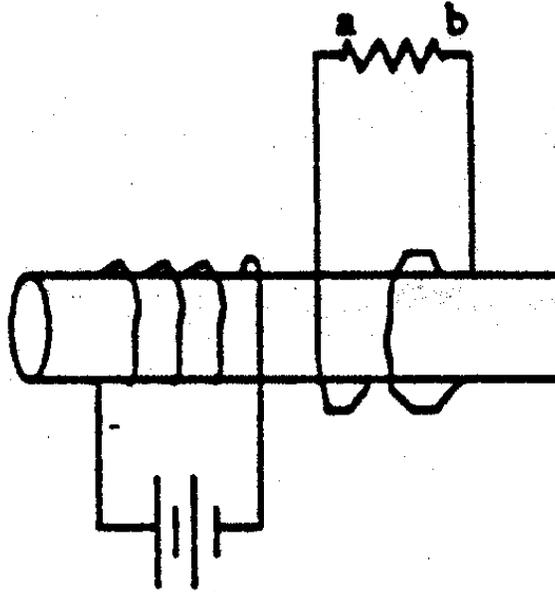**(f) A steady current flows in the circuit on the left.**




- A. from a to b
- B. from b to a
- \* C. zero
- D. it depends

39.

Determine whether point a or b is at a higher potential.

(a) Automobile Ignition System

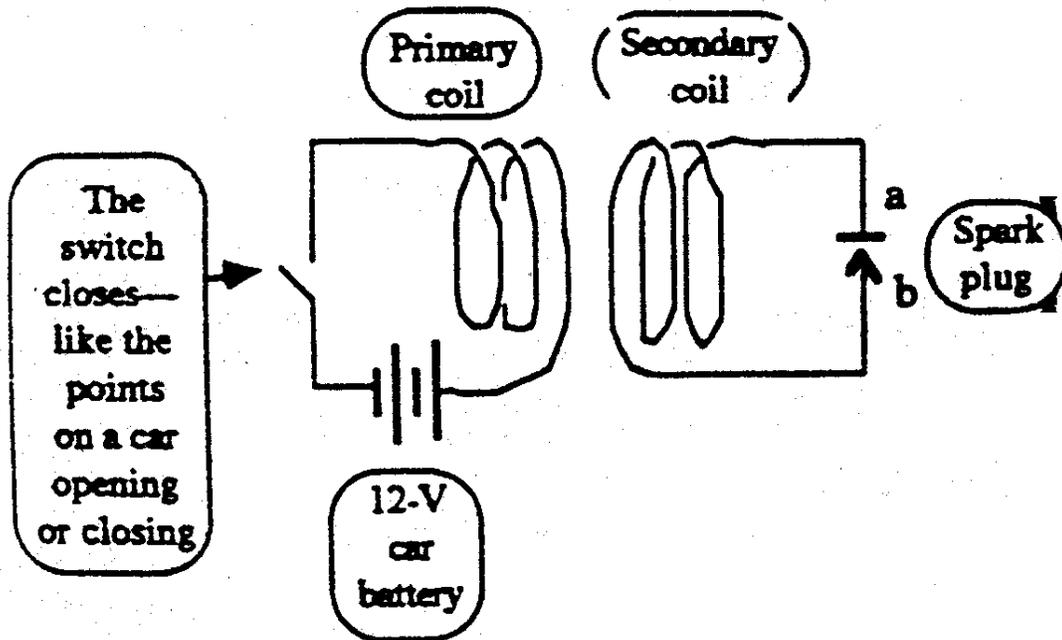


- \* A. point a
- B. point b
- C. same potential
- D. it depends

40.

Determine whether point a or b is at a higher potential.

**(b) Falling Bar Inductor**

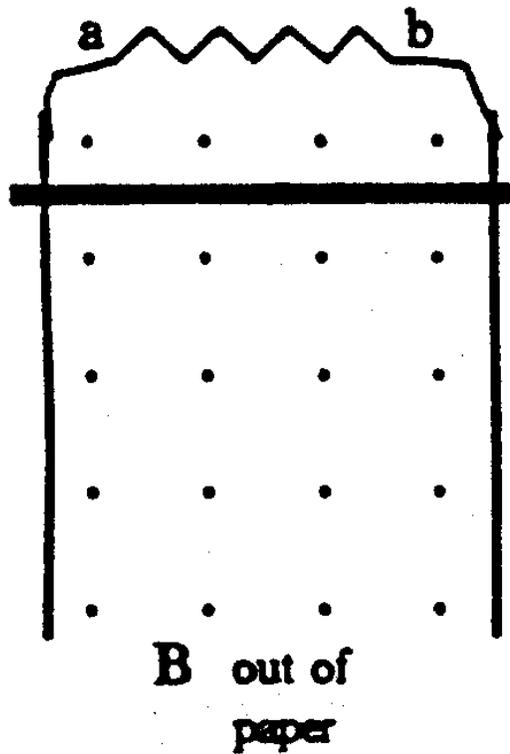**Determine the polarity of voltage across the resistor as the horizontal bar falls along the vertical side bars.**




- \* A. point a
- B. point b
- C. same potential
- D. it depends

41.

Determine whether point a or b is at a higher potential.

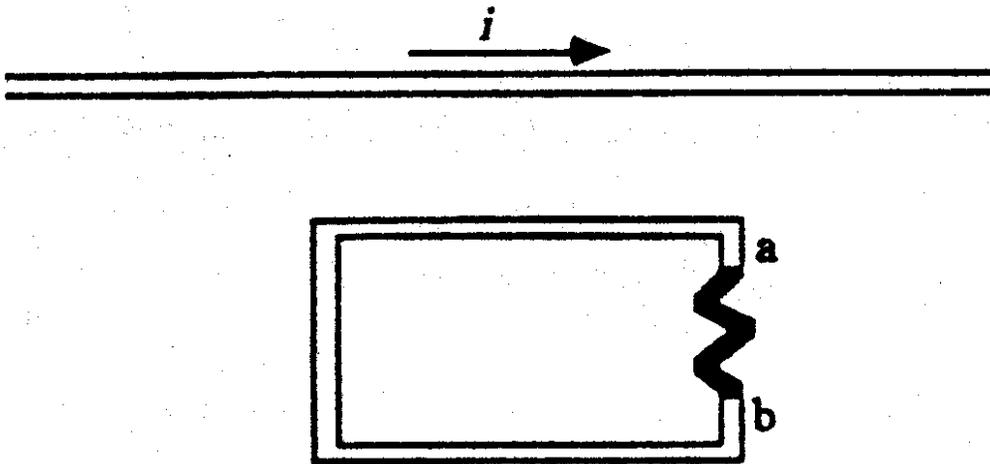**(c) Alternating Current Inductor**  
The current in the long straight wire, initially toward the right, reverses direction.




- \* A. point a  
B. point b  
C. same potential  
D. it depends

42.

Determine whether point a or b is at higher potential.

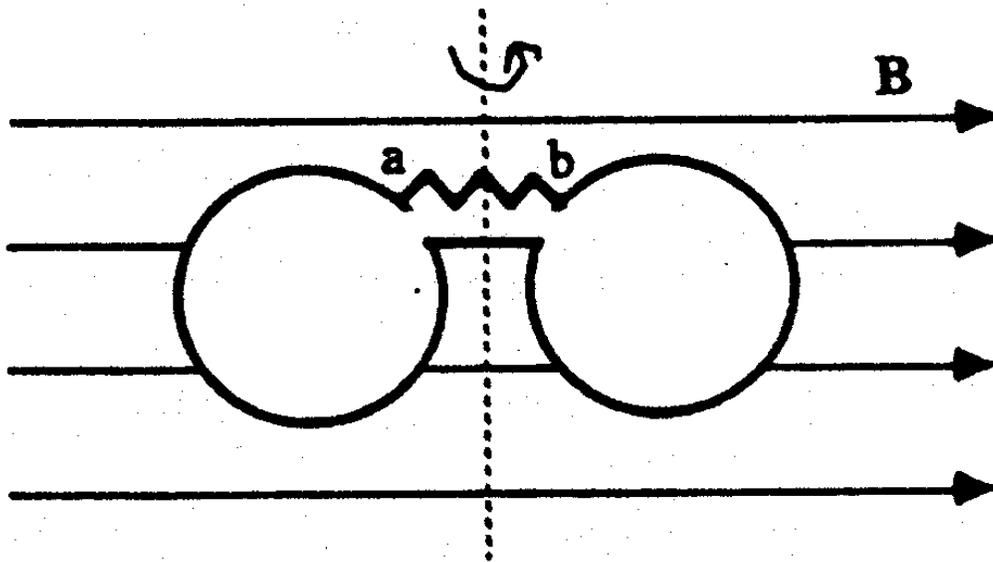
**(d) "Eyeglasses" Inductor**

The eyeglasses, initially in the plane of the magnetic field, are rotated  $90^\circ$  so that the rims now face in the direction of the magnetic field.



- \* A. point a
- B. point b
- C. same potential
- D. it depends

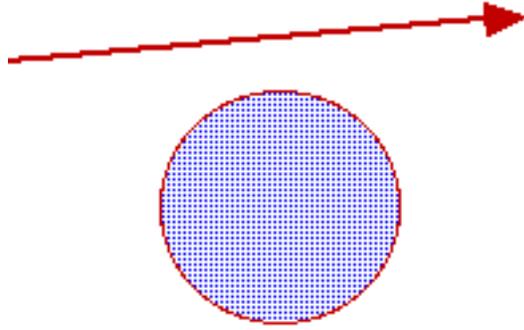43.  
A sphere of radius  $R$  is placed near a long straight wire carrying steady current  $I$ .  
The total magnetic flux passing through the surface of the sphere is:



A.  $m_0I$

B.  $m_0I/4\rho R^2$

C.  $4\rho R^2m_0I$

\* D. zero